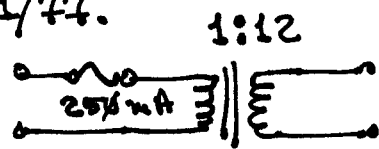


PP 3.1/77.



$$I_{\text{max}} = 25 \text{ mA}$$

$$I_s = \frac{N_p}{N_s} \times I_p$$

$$I_s = \frac{1}{12} \times 25 \text{ mA}$$

$$I_s = 2.08 \text{ mA}$$

PP 3.2/82.

$$N_p = 10 \quad N_s = 1 \quad \text{transformer turns}$$

$$V_p(\text{pk}) = 18 \text{ V}$$

$$V_s(\text{pk}) = \frac{N_s}{N_p} \times V_p(\text{pk})$$

$$V_s(\text{pk}) = \frac{1}{10} \times 18 \text{ V}$$

$$V_s(\text{pk}) = 1.8 \text{ V}$$

$$V_L(\text{pk}) = 18 \text{ V} - 0.7 \text{ V}$$

$$V_L(\text{pk}) = 17.3 \text{ V}$$

PP5.3/82.

$$V_T = 12V_{AC} \text{ transformer}$$

$$V_{S(pk)} = V_T / 0.707$$

$$V_{S(pk)} = 12V / 0.707$$


$$\boxed{V_{S(pk)} = 16.98V}$$

$$V_{L(pk)} = V_{S(pk)} - V_F$$

$$V_{L(pk)} = 16.98V - 0.7V$$

$$\boxed{V_{L(pk)} = 16.28V}$$

PP 3.4/83.

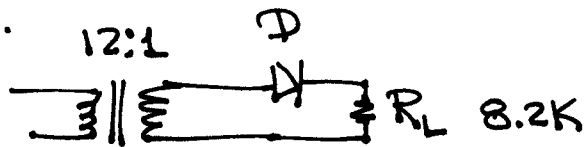

$$N_p = 12 \quad N_s = 1 \quad R_L = 8.2K$$

$$V_{S(\text{pk})} = \frac{N_p}{N_s} \times \frac{120V}{\sqrt{2}}$$

$$V_{S(\text{pk})} = \frac{1}{12} \cdot \frac{120V}{\sqrt{2}}$$

$$V_{S(\text{pk})} = 14.14V$$

$$V_{L(\text{pk})} = V_{S(\text{pk})} - V_F$$

$$V_{L(\text{pk})} = 14.14V - 0.7V$$


$$V_{L(\text{pk})} = 13.44V$$

$$I_{L(\text{pk})} = V_{L(\text{pk})} / R_L$$

$$I_{L(\text{pk})} = 13.44V / 8.2K$$

$$I_{L(\text{pk})} = 1.64mA$$

PP3.5/04.

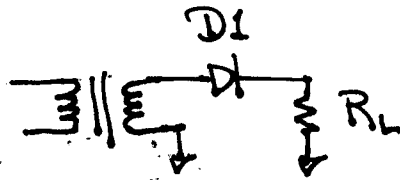

$$N_p = 14 \quad N_s = 1 \quad R_L = 8.2K$$

$$V_{P(\text{pk})} = V_{P(\text{rms})} / 0.707$$

$$V_{P(\text{pk})} = 120V / 0.707$$

$$\boxed{V_{P(\text{pk})} = 169.7V}$$

$$V_{S(\text{pk})} = \frac{N_s}{N_p} V_{P(\text{pk})}$$

$$V_{S(\text{pk})} = \frac{1}{14} \cdot V_{P(\text{pk})} = \frac{1}{14} \cdot 169.7V$$

$$\boxed{V_{S(\text{pk})} = 12.12V}$$

$$V_{L(\text{pk})} = 12.12V - 0.7V$$

$$\boxed{V_{L(\text{pk})} = 11.42V}$$

$$V_{\text{avg}} = V_{L(\text{pk})} / \pi$$

$$V_{\text{avg}} = 11.42V / 3.14$$

$$\boxed{V_{\text{avg}} = 3.64V}$$

PP 3.6/84.

half wave rectifier

$$V_{avg} = 24V$$

$$R_L = 2.2k\Omega$$

$$I_{avg} = V_{avg} / R_L$$

$$I_{avg} = 24V / 2.2k$$

$$I_{avg} = 10.9mA$$

PP 3.7/84.

half wave rectifier $48V_{ac}$ $R_L = 12k$

$$V_{S(pk)} = 48V_{ac} / 0.707 = 67.89V$$

$$V_{L(pk)} = V_{S(pk)} - 0.7V = 67.19V$$

$$I_{L(pk)} = V_{L(pk)} / R_L = \frac{67.19V}{12k} = 5.66mA$$

$$I_{avg} = I_{L(pk)} / \pi = 1.80mA$$

PP3.8/06.

negative half wave rectifier 30V_{ac} transformer

$$V_{s(pk)} = 30V_{ac} / 0.707 = 50.92V$$

$$V_{L(pk)} = V_{s(pk)} - 0.7V = 50.22V$$

$$V_{avg} = V_{L(pk)} / \pi = 50.22V / \pi = \frac{15.99}{\pi} = \underline{\underline{16.21V}}$$

$$V_{s(pk)} = -50.92V$$

$$V_{L(pk)} = -50.22V$$

$$V_{avg} = -16.21V$$

$$V_{avg} = -15.99V$$

calculator error =

human error



PP 3.9/89.

full wave rectified with 24 Vac center tapped transformer

$$V_{s(pk)} = \frac{24 V}{0.707}$$

$$V_{s(pk)} = 33.95 V$$

$$V_{L(pk)} = \frac{V_{s(pk)}}{2} - 0.7 V$$

$$V_{L(pk)} = 16.27 V$$

$$V_{avg} = 2 V_{L(pk)} / \pi$$

$$V_{avg} = 2 \cdot 16.27 V / \pi$$

$$V_{avg} = 10.36 V$$

PP3.10/90.

practice problem 3.9 has 2.2K load

$$I_{L(pk)} = \frac{V_{L(pk)}}{R_L} = \frac{16.27V}{2.2K}$$

$$I_{L(pk)} = 7.40 \text{ mA}$$

$$I_{avg} = V_{avg} / R_L$$

$$I_{avg} = 10.36V / 2.2K$$

$$I_{avg} = 4.71 \text{ mA}$$

pp 3.11/94.

bridge rectifier with 18 Vac transformer and 1.2k load

$$V_{S(\text{pk})} = \frac{18 V_{ac}}{0.707}$$

$$V_{S(\text{pk})} = 25.46V$$

$$V_{L(\text{pk})} = V_{S(\text{pk})} - 1.4V$$

$$V_{L(\text{pk})} = 25.46V - 1.4V$$

$$V_{L(\text{pk})} = 24.06V$$

$$V_{\text{avg}} = 2 V_{L(\text{pk})} / \pi$$

$$V_{\text{avg}} = 2 \cdot 24.06V / \pi$$

$$V_{\text{avg}} = 15.32V$$

$$I_{\text{avg}} = V_{\text{avg}} / R_L$$

$$I_{\text{avg}} = 15.32V / 1.2k$$

$$I_{\text{avg}} = 12.76 \text{ mA}$$

PP3.12/1pp.

using MDA2562 bridge rectifier with 12V_{ac} transformer
and load resistor 150 Ω.

$$V_{S(\text{pk})} = V_{ac} / 0.707$$

$$\boxed{V_{S(\text{pk})} = 16.97\text{V}}$$

$$V_{L(\text{pk})} = V_{S(\text{pk})} - 2V_F$$

$$V_{L(\text{pk})} = 16.97\text{V} - 2 \cdot 0.95\text{V}$$

$$\boxed{V_{L(\text{pk})} = 15.07\text{V}}$$

$$V_{\text{avg}} = 2 \cdot V_{L(\text{pk})} / \pi$$

$$V_{\text{avg}} = 2 \cdot 15.07\text{V} / \pi$$


$$\boxed{V_{\text{avg}} = 9.59\text{V}}$$

$$I_{\text{avg}} = V_{\text{avg}} / R_L$$

$$I_{\text{avg}} = 9.59\text{V} / 150\ \Omega$$

$$\boxed{I_{\text{avg}} = 64.6\text{mA}}$$

FP 3.14 / 14.

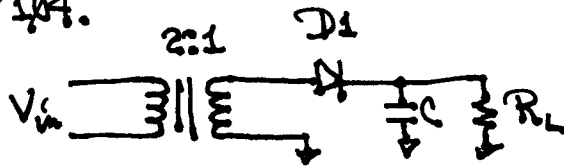

$$V_{in} = 170 \text{ V}_{pk}$$

$$V_{s(pk)} = \frac{N_s}{N_p} V_{in}$$

$$V_{s(pk)} = \frac{1}{2} \cdot 170 \text{ V}$$

$$\boxed{V_{s(pk)} = 85 \text{ V}}$$

$$I_{\text{surge}} = \frac{V_{s(pk)}}{R_w + R_B}$$

$$R_w = 0.5 \Omega \quad R_B = 8 \Omega$$

$$I_{\text{surge}} = \frac{85 \text{ V}}{0.5 \Omega + 8 \Omega}$$

$$I_{\text{surge}} = \frac{85 \text{ V}}{8.5 \Omega}$$

$$\boxed{I_{\text{surge}} = 10 \text{ A}}$$

PP 3.22/117.

using figure 3.48

$$V_s = 24V_{ac} \quad C = 47\mu F \quad R_s = 500\Omega \quad V_z = 10V \quad Z_z = 20\Omega \\ R_L = 5.1K$$

$$V_{s(pk)} = V_s / 0.707 = 33.95V$$

$$V_{pk} = V_{s(pk)} - 1.4V = 32.55V$$

$$I_B = \frac{V_{in} - V_z}{R_s} = \frac{32.55V - 10V}{R_s}$$

$$I_R = 45.1mA$$

$$V_r = \frac{I_R t}{C} = \frac{45.1mA \cdot 8.33ms}{47\mu F}$$

$$V_r = 799.3mV$$

$$V_{dc} = V_z = 10V$$

$$I_L = V_z / R_L = 10V / 5.1K$$

$$I_L = 1.96mA$$

$$V_{r(out)} = \frac{(Z_z || R_L)}{(Z_z || R_L + R_s)} \cdot V_r$$

$$V_{r(out)} = \frac{19.23}{19.23 + 500} \cdot 799.3mV$$

$$V_{r(out)} = 29.60mV$$