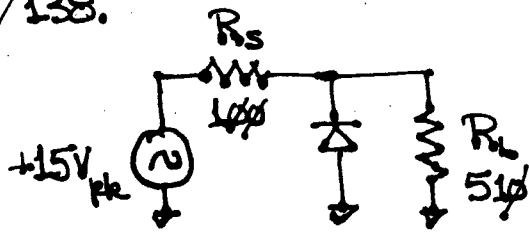


PP4.1/138.



$$V_L = \frac{R_L}{R_L + R_s} \cdot V_{in}$$

$$V_L = \frac{5\Omega}{10\Omega + 5\Omega} \cdot 15V$$

$$V_L = \frac{5\Omega}{15\Omega} \cdot 15V$$

$$V_L = 12.54V$$

PP4.2/139.

$$V_{in} = -15V_{pk}$$

$$V_{in} = -0.7V$$


$$V_{RS} = V_{in} + 0.7V$$

$$V_{RS} = -15V + 0.7V$$

$$V_{RS} = -14.3V$$

PP 4.3/14

positive shunt clipper

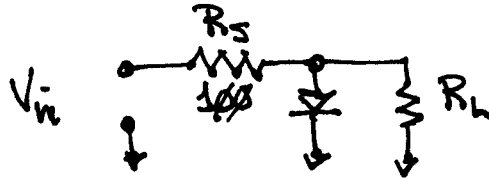

$$R_S = 100 \Omega \quad R_L = 1.1 \text{K} \quad V_{in} = \pm 12 \text{V}_{pk}$$

$$V_{in} = +12 \text{V}$$

$$V_{in} = V_{RS} + V_{RL}$$

$$V_{BS} = V_{in} - V_{RL}$$

$$V_{BS} = +12 \text{V} - 0.7 \text{V}$$

$$V_{RS} = 11.3 \text{V} \text{ when } V_{in} = +12 \text{V}$$

$$V_{RL} = +0.7 \text{V}$$

$$V_{in} = -12 \text{V}$$

$$V_{RL} = \frac{R_L}{R_L + R_S} \cdot V_{in}$$

$$V_{RL} = \frac{1.1 \text{K}}{1.1 \text{K} + 100} \cdot (-12 \text{V})$$

$$V_{RL} = -11.0 \text{V}_{pk}$$

PP4.5/147.

clamped $R_{D1} = 8 \Omega$ $C_1 = 4.7 \mu\text{F}$ $R_L = 1.2\text{K}$

$$\tau_c = 5(R_{D1} C_1)$$

$$\tau_c = 5 \cdot 8 \Omega \cdot 4.7 \times 10^{-6} \text{ F}$$

$$\tau_c = 188 \mu\text{s}$$

$$\tau_D = 5(R_L C_1)$$

$$\tau_D = 5 \cdot 1.2\text{K} \cdot 4.7 \times 10^{-6} \text{ F}$$

$$\tau_D = 6 \times 10^3 \cdot 4.7 \times 10^{-6} \text{ s}$$

$$\tau_D = 28.2 \times 10^{-3} \text{ s}$$

$$\tau_D = 28.2 \text{ ms}$$