

PP 5.1/179.

$$L = 3.3 \text{ mH} = 3.3 \times 10^{-3} \text{ H}$$

$$C_c = 51 \text{ pF} = 51 \times 10^{-12} \text{ F}$$

$$V_R = 4 \text{ V} \quad C_R = 1.8 \text{ pF} \quad 4 \text{ V} \leq V_R \leq 10 \text{ V}$$

$$f_{4V} = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{3.3 \times 10^{-3} \cdot 51 \times 10^{-12}}}$$

$$f_{20V} = \frac{1}{2\pi\sqrt{1.68 \times 10^{-13}}}$$

$$f_{4V} = 387.9 \text{ kHz}$$

$$C_{10V} = \frac{C_c}{C_R} = \frac{51 \text{ pF}}{1.8} = 28.3 \text{ pF}$$

$$f_{10V} = \frac{1}{2\pi\sqrt{LC}}$$

$$f_{10V} = \frac{1}{2\pi\sqrt{3.3 \times 10^{-3} \cdot 28.3 \times 10^{-12}}}$$

$$f_{10V} = \frac{1}{2\pi\sqrt{9.34 \times 10^{-14}}}$$

$$f_{10V} = 526.8 \text{ kHz}$$

PP 5.2/18%

Re-do PP5.1 with $C_R = 1.07$

$$V_R = 4V$$

$$f_{1V} = 387.9 \text{ kHz}$$

as nothing has changed.

NOTE: The frequency changes as $\sqrt{C_R}$. I figured this out and you can too!

If $C_R = 1.8$ (as in PP5.1)

$$f_{10V} = f_{1V} \times \sqrt{C_R} = 387.9 \text{ kHz} \times 1.34 = 520.4 \text{ kHz}$$

For $C_R = 1.07$

$$f_{10V} = f_{4V} \times \sqrt{C_R}$$

$$f_{10V} = 387.9 \text{ kHz} \times \sqrt{1.07}$$

$$f_{10V} = 387.9 \text{ kHz} \times 1.034$$

$$f_{10V} = 401.25 \text{ kHz}$$

Frequency range is reduced with lower C_R values.