

NOTES & PROBLEM SETS
de
K7QO

INTRODUCTORY ELECTRONIC DEVICES & CIRCUITS
SIXTH EDITION
Conventional Flow Version

by
ROBERT T. PAYNTER

MAR 24, 2017 →

CHAPTER 1 NOTES

CHAPTER 1 — Fundamental Solid State Principles

proton +1 charge 1.673×10^{-24} g

neutron 0 charge 1.675×10^{-24} g

electron -1 charge 9.11×10^{-28} g

+1 charge = 1.602×10^{-19} C

semiconductor materials Si, Ge and C

conductors $E_g = 0.4$ eV

semiconductors $E_g = 1.1$ eV

insulators $E_g = 1.8$ eV


bias - voltage applied to obtain a desired mode of operation

forward biased diode $V_F \approx 0.7$ V (Si)

$V_F \approx 0.3$ V (Ge)

CHAPTER 2 NOTES

CHAPTER 2 — Diodes

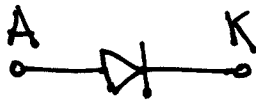schematic symbol anode  cathode

note: diode conducts fully when $V_F = 0.7V$ for Si
and $0.3V$ for Ge

it is conducting when voltage is smaller!!
i see lots of hams online screw this one up.


model — representation that demonstrates one or more characteristics of a component or circuit

ideal diode model — simple switch

practical diode model — practical model for analyzing circuit

complete diode model — used for computer simulations

practical diode model

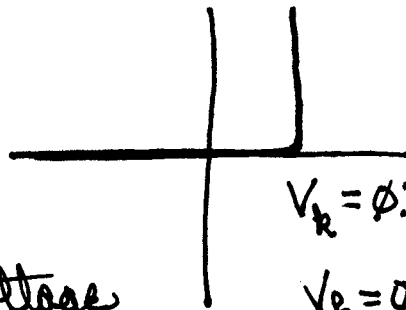

V_k — knee voltage

$$V_k = 0.7V \text{ (Si)}$$

$$V_k = 0.3V \text{ (Ge)}$$

$$\text{percentage of error [\%]} = \frac{[x - x']}{x'} \times 100 \quad (2.3)$$

BOOK IS WRONG !!


google it — 'percentage of error'

do calculations without absolute value operation

problem notation

PP 2.1/24.

practice problem 2.1 on page 24

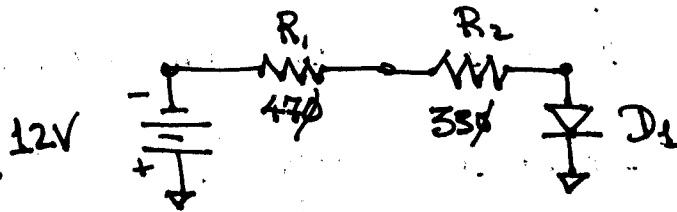


$$V_{R1} = 0.7V$$

$$V_{R2} = 0.7V$$

$$V_{D1} = -12V \text{ from anode to cathode}$$

$$I = 0.5 \mu A \text{ for ideal diode model}$$

PP 2.2/24.

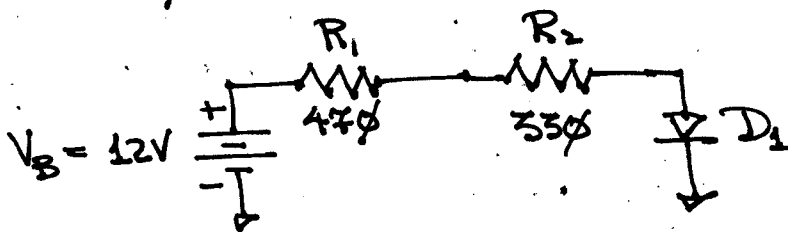


$$I_T = \frac{V_B}{R_1 + R_2}$$

$$I_T = \frac{12V}{47\Omega + 33\Omega}$$

$$I_T = \frac{12V}{80\Omega}$$

$$I_T = 150 \text{ mA}$$

PP 2.3/27.

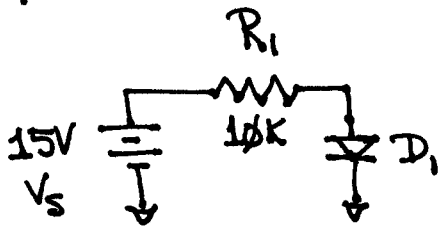

$$I = \frac{V_s - V_F}{R_1}$$

$$I = \frac{15V - 0.7V}{10K}$$


$$I = \frac{14.3V}{10K}$$

$$I = 1.43mA$$

$$V_{R_1} = I \times R_1$$

$$V_{R_1} = 14.3V$$

PP 2.4/27.

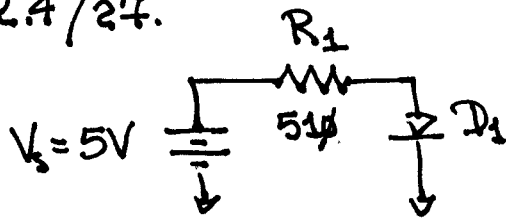


$$I = \frac{V_s - V_F}{R_1}$$

$$I = \frac{5V - 0.7V}{510\Omega}$$

$$I = \frac{4.3V}{510\Omega}$$

$$I = 8.43mA$$

PP2.5/28.

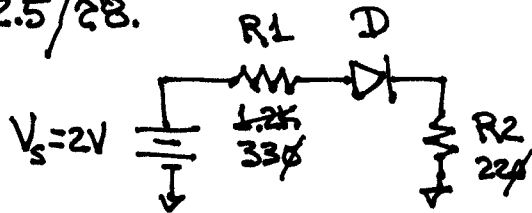


$$I = \frac{V_s - V_f}{R_1 + R_2}$$

$$I = \frac{2.0V - 0.7V}{33\Omega + 22\Omega}$$

$$I = \frac{1.3V}{55\Omega}$$

$$I = 2.36 \text{ mA}$$

PP2.6/28

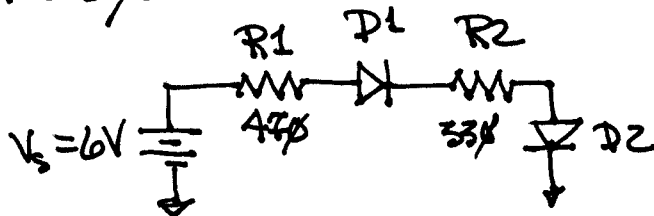


$$I = \frac{V_s - V_{D1} - V_{D2}}{R_1 + R_2}$$

$$I = \frac{6.0V - 0.7V - 0.7V}{47\Omega + 33\Omega}$$

$$I = \frac{4.6V}{80\Omega}$$

$$I = 5.75 \text{ mA}$$

PP 2.7/29.

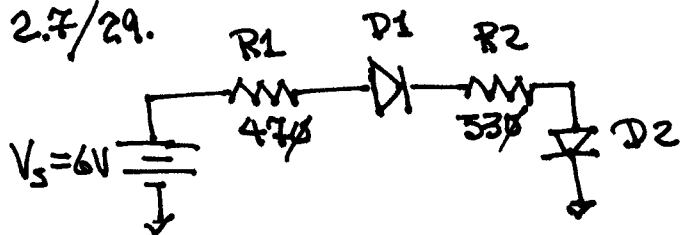

using ideal diode model

$$I = \frac{V_s - V_{D1} - V_{D2}}{R1 + R2}$$

$$I = \frac{6.0V - 0.0V - 0.0V}{47\Omega + 33\Omega}$$

$$I = \frac{6.0V}{80\Omega}$$

$$I = 7.5 \text{ mA}$$

using correct percentage error formula

$$PE = \frac{I - I'}{I'} \times 100\%$$

$$PE = \frac{7.5 \text{ mA} - 5.75 \text{ mA}}{5.75 \text{ mA}} \times 100\%$$

$$PE = 30.4\%$$

ideal model value too large

using wrong percentage error formula in book

$$PE = \frac{|I - I'|}{I} \times 100\%$$

$$PE = \frac{7.5 - 5.75}{7.5} \times 100\%$$

$$PE = 23.3\%$$

value too low

PP2.8/31.

$$V_{pk} = 175V$$

$$V_{RRM} = 1.2 \times V_{pk}$$

$$V_{RRM} = 1.2 \times 175V$$


$$V_{RRM} = 210V$$

	<u>peak reverse voltage</u>
1N4001	50V
1N4002	100V
1N4003	200V
1N4004	400V
1N4005	600V
1N4006	800V
1N4007	1000V

diodes that can be used are

1N4004
1N4005
1N4006
1N4007

PP 29/32.

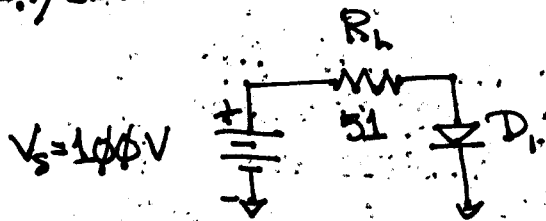

$$I_F = \frac{V_s - V_F}{R_L}$$

$$I_F = \frac{100.0V - 0.7V}{51\Omega}$$

$$I_F = 1.95A$$


$$I_D = 1.2 \times I_F$$

$$I_D = 1.2 \times 1.95A$$

$$I_D = 2.34A$$

minimum average current rating for diode

PP 2.14/33.

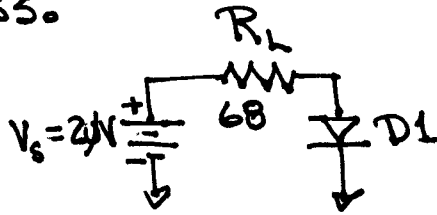

$$I_F = \frac{V_s - V_F}{R_L}$$

$$I_F = \frac{2V - 0.7V}{68\ \Omega}$$

$$I_F = \frac{1.3V}{68\ \Omega}$$

$$I_F = 273.5\ \text{mA}$$

$$P_F = (0.2735\ \text{A})(0.7\ \text{V})$$

$$P_F = 191.5\ \text{mW}$$

$$P_D = 1.2 \times 191.5\ \text{mW}$$

$$P_D = 230\ \text{mW}$$

minimum rating for diode

PP 2.11/34.

diode rating $P_D = 500 \text{ mW}$

$$I_D = 750 \text{ mA}$$

$$V_F = 0.7 \text{ V}$$

$$P_D = I_D \times V_F$$

$$P_D = 750 \text{ mA} \times 0.7 \text{ V}$$

$$\boxed{P_D = 525 \text{ mW}} > 500 \text{ mW, thus } P_D \text{ exceeded}$$

PP 2.12/36.

$$R_B = 8\Omega \quad I_D = 12\text{mA}$$

$$V_F = V_B + I_D R_B$$

$$V_F = 0.7\text{V} + 12\text{mA} \cdot 8\Omega$$

$$V_F = 0.7\text{V} + 0.096\text{V}$$

$$\boxed{V_F = 0.796\text{V}}$$

PP 2.13/49.

zener diode $P_D = 1W$

$$V_Z = 27V$$

$$I_{ZM} = P_D / V_Z$$

$$I_{ZM} = 1W / 27V$$

$$I_{ZM} = 37.1 \text{ mA}$$

PP 2.14/50.

$T = 125^\circ C$ operating temperature for zener

$$\text{derating value} = (4 \text{ mV}/^\circ C) (125^\circ C - 75^\circ C)$$

$$\text{derating value} = 200 \text{ mV}$$

$$P_D = 500 \text{ mW} - 200 \text{ mW}$$

$$P_D = 300 \text{ mW}$$

PP 2.15/52.

$$V_z = 75V \text{ for zener diode}$$

$$P_D = 4W$$

using figure 2.34 :

1N5374A

zener to use in application

PP 2.16/53.

$$V_z = 6.8V$$

$$I_z = 175 \text{ mA}$$

$$P_D = V_z \cdot I_z$$

$$P_D = 6.8V \cdot 175 \text{ mA}$$

$$P_D = P_D = 1.19W$$

1N5921A @ 1.5W
1N5342A @ 5W

← 6.8V zeners could be used

PP 2.17/56.

$$1.4V \leq V_F \leq 1.8V$$

LED voltage range

$$I_F = 12 \text{ mA}$$

$$V_{pk} = 14V$$

$$R_S = \frac{V_{pk} - V_F}{I_F}$$

$$R_S = \frac{14V - 1.4V}{12 \text{ mA}}$$

use minimum V_F

$$R_S = 1050 \Omega$$


calculated value

1.5 K for 10% tolerance

1.3 K for 2% and 5% tolerance


from appendix A, page 928.

1/64.

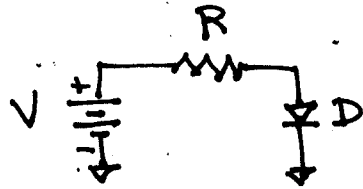


forward biased diode

2/64.

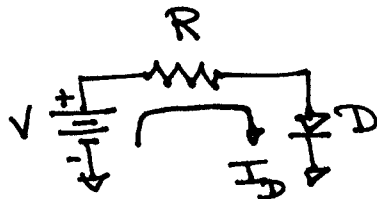

current direction, conventional flow


3/64.

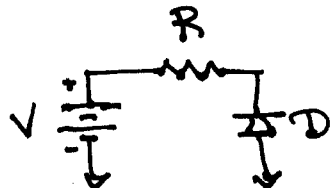

reverse biased diode


4/64.

(2)

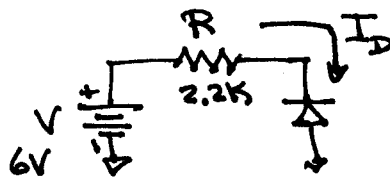


I_D is very small
reverse bias applied to diode
for ideal model, $I_D = 0,0 \mu A$

(b)

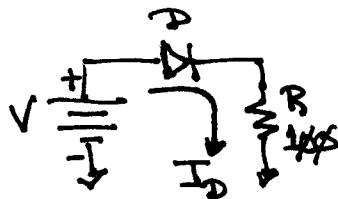

forward biased

(c)

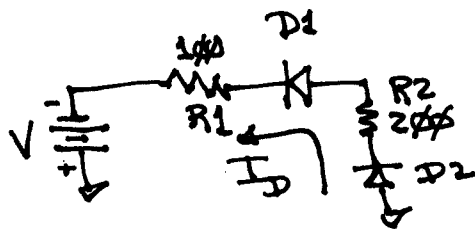

both diodes forward biased

5/64.


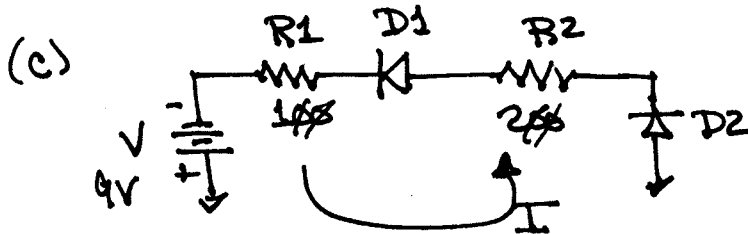
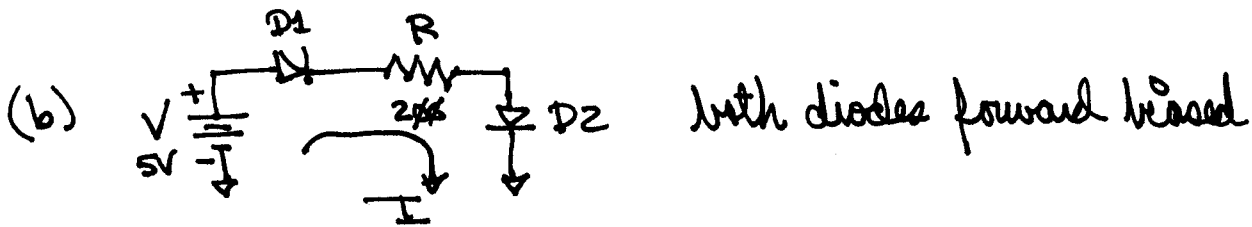
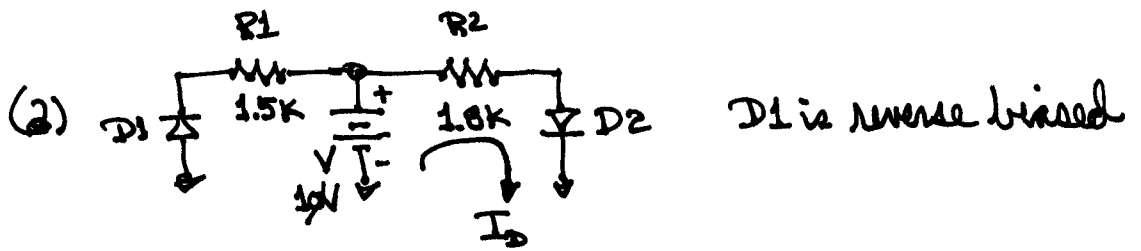


Diagram shows that maybe, just maybe, D2 should be voltage source of 6V

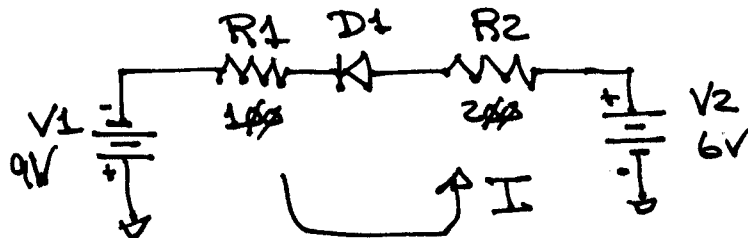

$V_1 > V_2$, thus D1 is forward biased

14/65.

$$V' = 12.8V \quad \text{calculated voltage}$$

$$V = 13.2V \quad \text{measured voltage}$$

$$E = \frac{V - V'}{V'} \times 100\%$$

$$E = \frac{13.2V - 12.8V}{12.8V} \times 100\%$$

$$E = \frac{0.4}{12.8} \times 100\%$$

$$E = 0.031 \times 100\%$$

$$\boxed{E = 3.1\%} \quad \text{percentage error}$$

since positive, measured value is higher than calculated value

15/65.

$$I' = 750 \mu A$$

$$I = 880 \mu A$$


$$E = \frac{I - I'}{I'} \times 100\%$$

$$E = \frac{880 \mu A - 750 \mu A}{750 \mu A} \times 100\%$$

$$E = \frac{130 \mu A}{750 \mu A} \times 100\%$$

$$\boxed{E = 17.3\%}$$

17/65.

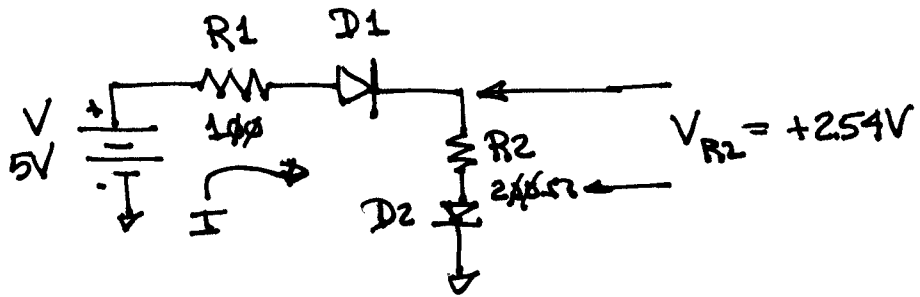

$$I = \frac{V - V_{D1} - V_{D2}}{R_1 + R_2}$$

$$I = \frac{5.0V - 0.7V - 0.7V}{100\ \Omega + 200\ \Omega}$$

$$I = \frac{3.6V}{300\ \Omega}$$

$$I = 12\text{ mA}$$

$$V'_{R_2} = I \cdot R_2$$

$$V'_{R_2} = 12\text{ mA} \cdot 200\ \Omega$$

$$V'_{R_2} = 2.4V$$

$$E = \frac{V - V'}{V'} \times 100\%$$


$$E = \frac{2.54V - 2.4V}{2.54V} \times 100\%$$

$$E = \frac{0.14V}{2.54V} \times 100\%$$

$$E = 5.5\%$$

26/66.

Si diode

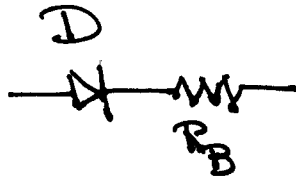

$$I = 10 \text{ mA}$$

$$R_B = 5 \Omega$$

what is V_F

$$V_B = I \cdot R_B$$


$$V_B = 10 \text{ mA} \cdot 5 \Omega$$

$$V_B = 0.05 \text{ V}$$

$$V_F = 0.7 \text{ V} + V_B$$

$$V_F = 0.75 \text{ V}$$

4/68.

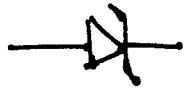

$D1$

$$V_z = 24V$$

$$P_{D(max)} = 10W$$

$$I_{zm} = ?$$


assume operation at $\frac{1}{2} P_{D(max)}$

$$I_{zm} = \frac{P}{V_z}$$

$$I_{zm} = 5W / 24V$$

$$I_{zm} = 208mA$$

52/69.

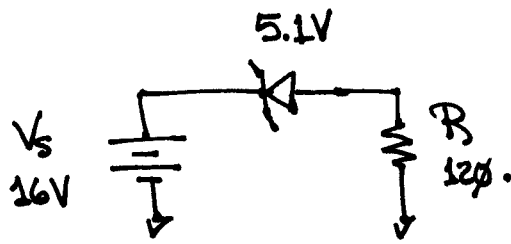

$$V_R = V_s - V_Z$$

$$V_R = 16V - 5.1V$$


$$V_R = 10.9V$$

$$I = \frac{V_R}{R}$$

$$I = \frac{10.9V}{120\Omega}$$

$$I = 90.8 \text{ mA}$$

53/69.

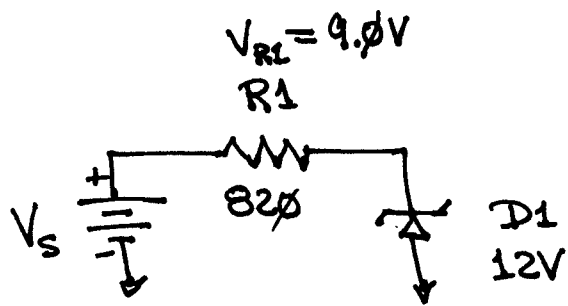

$$P_{D1} = ?$$

$$I = V_{R1} / R1$$

$$I = 9.0V / 82\Omega$$

$$I = 10.98 \text{ mA}$$

$$P = I \cdot V_{D1}$$

$$P = 10.98 \text{ mA} \cdot 12V$$

$$P = 132 \text{ mW}$$